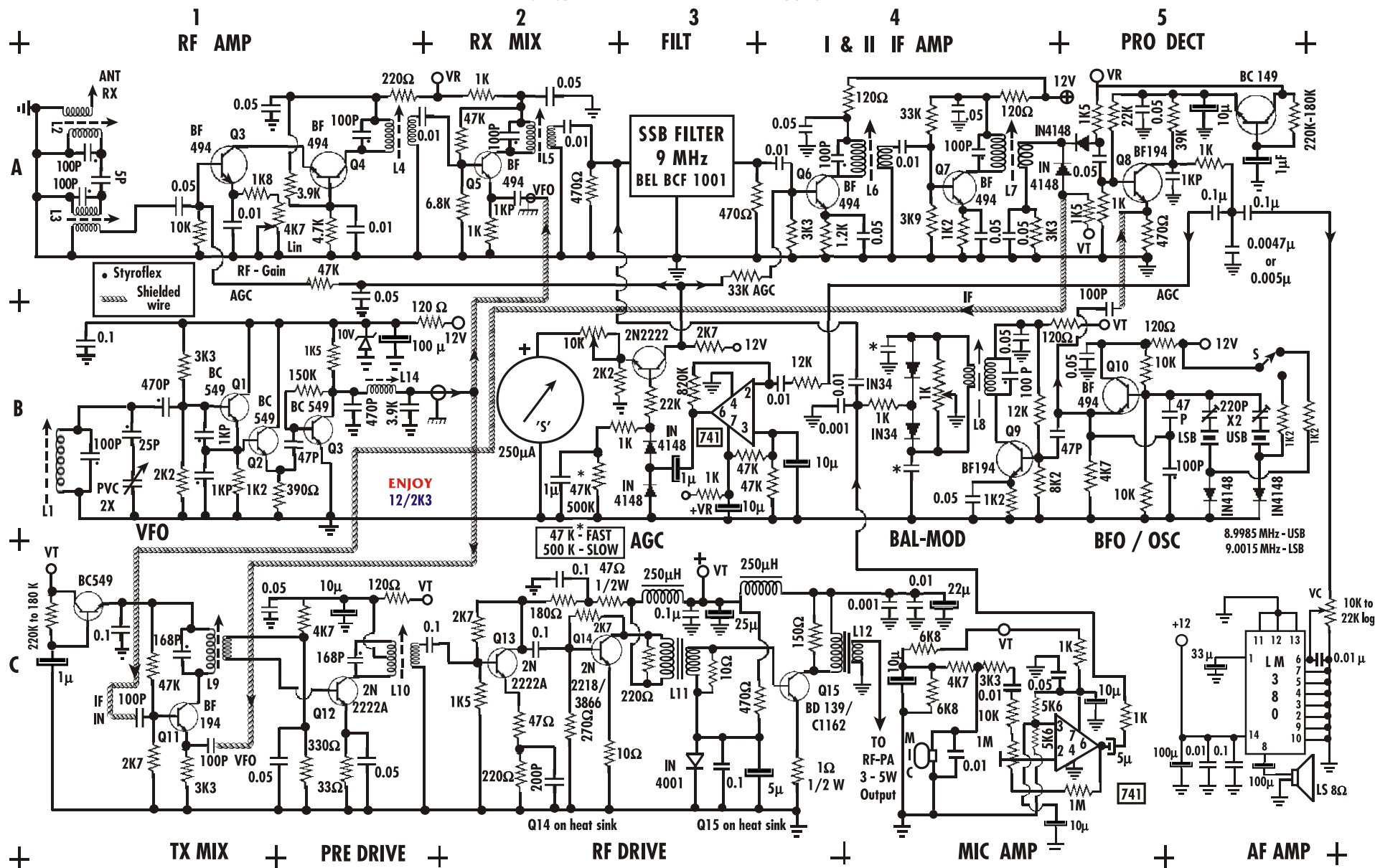



HF TXVER RM-96 / VER.1

CIRCUIT REDRAWN BY HARI - VU3NSH




Connect 150 PF parallel with 220 ohms at L11 and 150 ohms at L12 .


RM96 BLOCK DIAGRAM

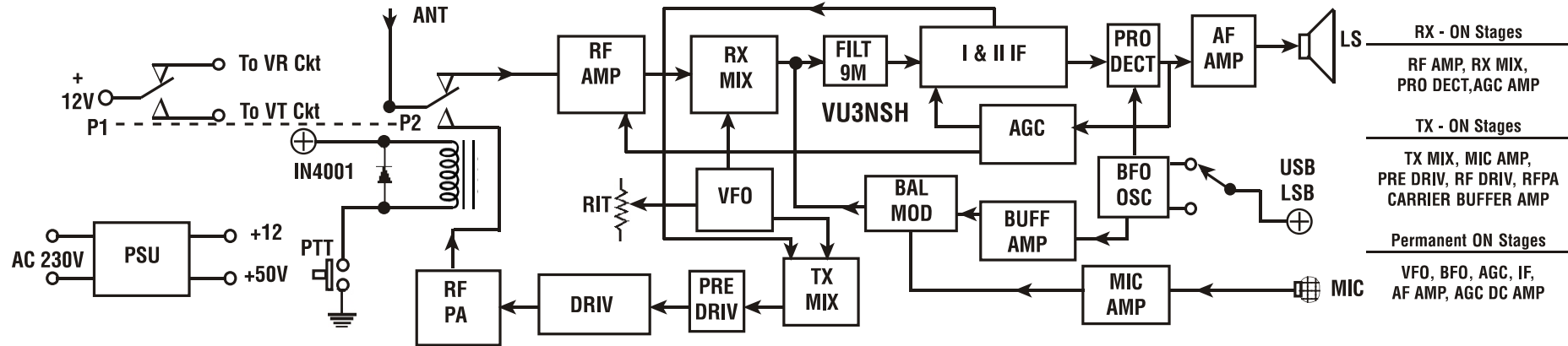


POWER SUPPLY

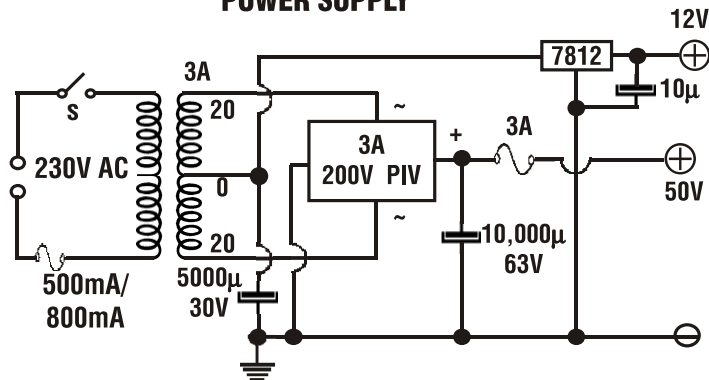

RF PA


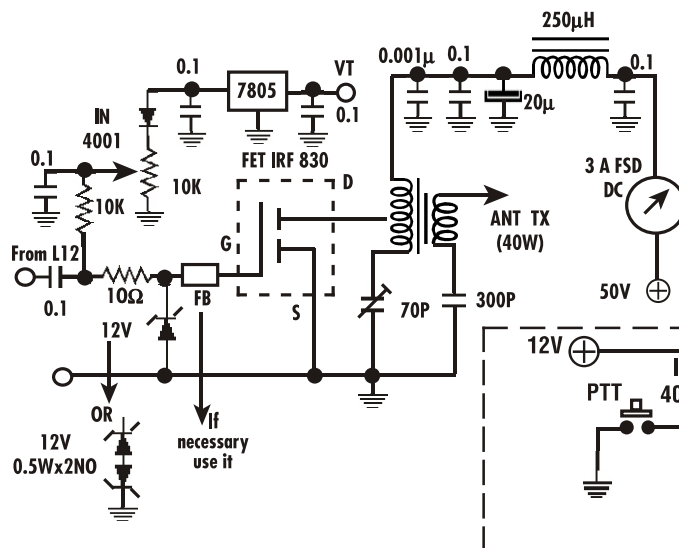


PTT & RELAY CIRCUIT

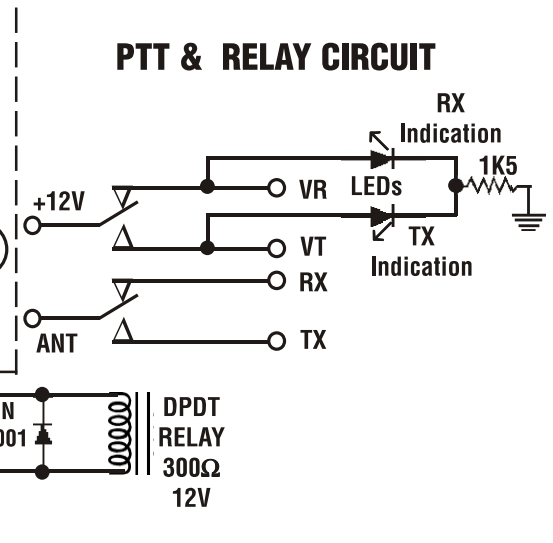

RM 96 SSB TRANSCEIVER - COIL WINDING DATA

By N.S. Harisankar VU3NSH

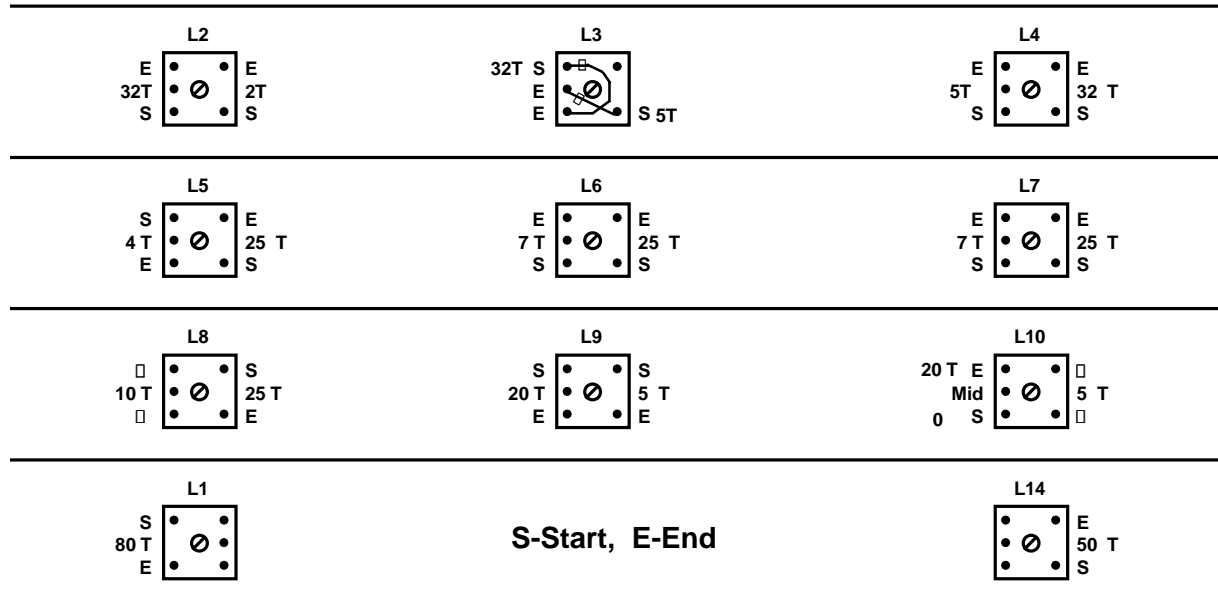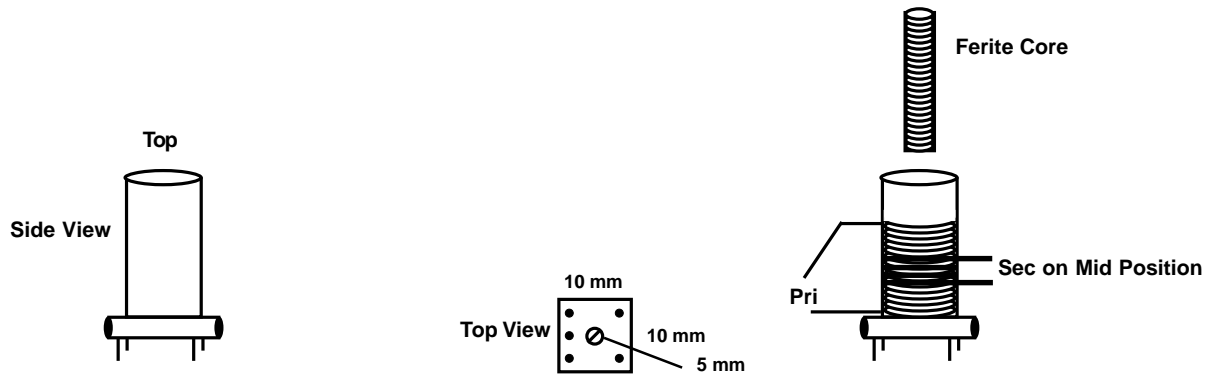

All coils are closed winded, more turns at first and less turns at mid. In figure, Left and right pins positions as on PCB Top side. All coil winding wires is of 36 SWG. Above mentioned all coils are IFT type and 5mm coil former with 10mm squire base and 5 pins and ferrite slug and can

For IFT formers, help may be available from VU2VIT, VU2SDN & VU2PTR.

SHOPPING LIST FOR RM 96 HF TXVER

PART- III

by N.S. Harisankar VU3NSH

BPF & RF Amp		1k5 \square $\frac{1}{4}$ W	1 Nos.	12 k \square $\frac{1}{4}$ W	1 No.
L2, L3 & L4		BF494	2 Nos.	33 k \square $\frac{1}{4}$ W	1 No.
100 PF - Styroflex	3 Nos.	1N4148	2 Nos.	47 k \square / 500k \square	1+1 Nos.
4.7 PF or 5PF	1 No.			10 k Preset	1 No.
0.047 \square F	2 Nos.	Pro. Dect			
0.01 \square F	3 Nos.	0.047 \square F	2 Nos.	741 IC	1 No.
10K \square $\frac{1}{4}$ W	1 No.	0.001 \square F	1 No.	1N4148	2 Nos.
1k8 \square $\frac{1}{4}$ W	1 No.	0.1 \square F	2 Nos.	2N2222	1 No.
3k9 \square $\frac{1}{4}$ W	1 No.	0.0047 \square F	1 No.	250 \square A - VU meter	1 No.
4k7 \square $\frac{1}{4}$ W	1 No.	10 \square F 25V	1 No.	BFO / OSC	
220 \square $\frac{1}{4}$ W	1 No.	1 \square F 25V	1 No.	0.047 \square F	1 No.
4k7 Pot, Lin	1 No.	22 k \square $\frac{1}{4}$ W	1 No.	100PF-Styroflex	1 No.
BF494	2 Nos.	39 k \square $\frac{1}{4}$ W	1 No.	47 PF-Styroflex	1 No.
RX MIX & Filter		470 \square $\frac{1}{4}$ W	1 No.	30 PF Trimmer	2 Nos.
L5		1 k \square $\frac{1}{4}$ W	2 Nos.	100 PF	1 No.
100PF-Styroflex	1 No.	220k to 180k $\frac{1}{4}$ W	1 No.	120 \square $\frac{1}{4}$ W	1 No.
0.047 \square F	1 No.	BF 494	1 No.	10k \square $\frac{1}{4}$ W	2 Nos.
0.01 \square F	2 Nos.	BC 547	1 No.	4k7 \square $\frac{1}{4}$ W	1 No.
0.001 \square F	1 No.	AF Amp			
47 k \square $\frac{1}{4}$ W	1 No.	33 \square F 25V	1 No.	1k2 Ω $\frac{1}{4}$ W	2 Nos.
1 k \square $\frac{1}{4}$ W	2 No.	100 \square F 25V	2 Nos.	BF 494	1 No.
6 k8 \square $\frac{1}{4}$ W	1 No.	0.01 \square F	2 Nos.	1N4148	2 Nos.
470 \square $\frac{1}{4}$ W	2 Nos.	0.001 \square F	1 No.	LSB/USB Crystal	
BEL - SSB Filter 9MHZ		LM 380 IC	1 No.	BEL-9.0015&8.9985	1+1 Nos.
9 MHZ (BCF 1001)	1 No.	8 \square 1W SP	1 No.	VFO	
BF494	1 No.	10k to 22k Pot.Log	1 No.	L1 & L 14	
I & II IF Amp		AGC			
L6, L7		0.01 \square F	1 No.	100 PF-Styroflex	1 No.
100 PF-Styroflex	2 Nos.	1 \square F 25V	2 Nos.	470 PF-Styroflex	2 Nos.
0.047 \square F	5 Nos.	10 \square F 25 V	2 Nos.	1k PF-Styroflex	2 Nos.
0.01 \square F	1 No.	1 k \square $\frac{1}{4}$ W	2 Nos.	47 PF-Styroflex	1 No.
120 \square $\frac{1}{4}$ W	2 Nos.	2 k2 \square $\frac{1}{4}$ W	1 No.	3k9 PF-Styroflex	1 No.
3 k3 \square $\frac{1}{4}$ W	2 Nos.	2 k7 \square $\frac{1}{4}$ W	1 No.	0.1 \square F	1 No.
1 k2 \square $\frac{1}{4}$ W	2 Nos.	22 k \square $\frac{1}{4}$ W	1 No.	100 \square F 25 V	1 No.
3k9 \square $\frac{1}{4}$ W	1 No.	820 k \square $\frac{1}{4}$ W	1 No.	BC 549	3 Nos.
33k \square $\frac{1}{4}$ W	1 No.	47 k \square $\frac{1}{4}$ W	3 Nos.	10V-400mw Zener	1 No.
				120 \square $\frac{1}{4}$ W	1 No.
				3k3 \square $\frac{1}{4}$ W	1 No.
				2k2 \square $\frac{1}{4}$ W	1 No.

1k2 \square ¼ W	1 No.	4.7 \square F 25 V	1 No.	BF 494	1 No.
1k5 \square ¼ W	1 No.	1 k \square ¼ W	2 Nos.	2N2222	1 No.
150k \square ¼ W	1 No.	1 M \square ¼ W	1 No.		
390 \square ¼ W	1 No.	10 k \square ¼ W	1 No.	RF Driv	
2X - Gang + 25 PF or 20 PF Gang		6 k8 \square ¼ W	2 Nos.	L ₁₁ & L ₁₂	
BAL. MOD		4 k7 \square ¼ W	1 No.	200 PF - Styroflex	1 No.
L8		3 k3 \square ¼ W	1 No.	150 PF - Styroflex	1 No.
100 PF - Styrolex	1 No.	10 k \square ¼ W	1 No.	180 PF - Styroflex	1 No.
47 PF	1 No.	5 k6 \square ¼ W	2 Nos.	0.1 \square F	4 Nos.
0.047 \square F	2 Nos.	1 M \square Preset	1 No.	0.01 \square F	1 No.
0.01 \square F	1 No.	741 IC	1 No.	25 \square F / 22 \square F - 25 V	2 Nos.
0.001 \square F	1 No.	2 Pin con - MIC	1 No.	4.7 \square F - 25 V	1 No.
30PF Trimmer	2 Nos.	TX - MIX & RF Pre.Driv.		47 \square ½ W	1 No.
12 k \square ¼ W	1 No.	L ₉ & L ₁₀		1 \square ½ W	1 No.
120 \square ¼ W	1 No.	168 PF - Styroflex	2 Nos.	470 \square ½ W	1 No.
8 k2 \square ¼ W	1 No.	100 PF	2 Nos.	10 \square ¼ W	1 No.
1 k2 \square ¼ W	1 No.	0.047 \square F	3 Nos.	220 \square ¼ W	2 Nos.
1 k \square ¼ W	1 No.	0.1 \square F	2 Nos.	47 \square ¼ W	1 No.
1 k Preset	1 No.	1 \square F 25 V	1 No.	1k5 \square ¼ W	1 No.
1N34 or 1N4148	2 Nos.	10 \square F 25 V	1 No.	2k7 \square ¼ W	2 Nos.
MIC Amp		47 k \square ¼ W	1 No.	270 \square ¼ W	1 No.
0.047 \square F	1 No.	2k7 \square ¼ W	1 No.	180 \square ¼ W	1 No.
0.01 \square F	2 Nos.	3k3 \square ¼ W	1 No.	150 \square ¼ W	1 No.
10 \square F 25 V	3 Nos.	47 k \square ¼ W	1 No.	2N2222	1 No.
		120 \square ¼ W	1 No.	2N2218 / 2N3866	1 No.
		330 \square ¼ W	1 No.	BD139/C1162	1 No.
		180 k to 220 k	1 No.	1N4007	1 No.
				250 \square H RFC	2 Nos.

Heat sink for 2N2218 & BD 139 1 +1 Nos. RFC - 20T - 28 SWG on FT 37-43 or T-O5 HFA / Balun

Ref circuit & coil Data on Back issue (1) HRN - Jan - Mar 2003, (2) HRN - April-June 2003

For getting technical support use forums in "www.hamradioindia.org".

On air 40m band you can discuss with VU2ETO, VU2GIP, VU2VJY, VU2PTR, VU2HRS, VU2POP, VU2BFO VU2GIP - OM Gopi has made 24 numbers of RM96 transceivers.

For getting 14 MHz (20m band) transceiver kit contact VU2IF. The kit named ATS1 is having a complete assembling manual, circuit and component list. The PCB is epoxy with all components marked. The kit is having all IFTs and coils.

For frequency counter PCBs and PUSH-PULL RF AMP for this projects are available with me.